

Assignment-3 (CS 232) by Utkarsh Ranjan

1-bit Half Adder

Components

1 XOR gate, 1 And gate

Description


- 2 Inputs :- two bits (A,B)
- 2 Outputs :- two bits (Carry, add)

Carry = A + B; Sum = A xor B;

- To construct the Xor Gate - 1 And gate, 1 Or gate and 1 Nand gate were used

A	B	Sum	Carry
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1

OnebitHalfAdd:HalfAddInst1

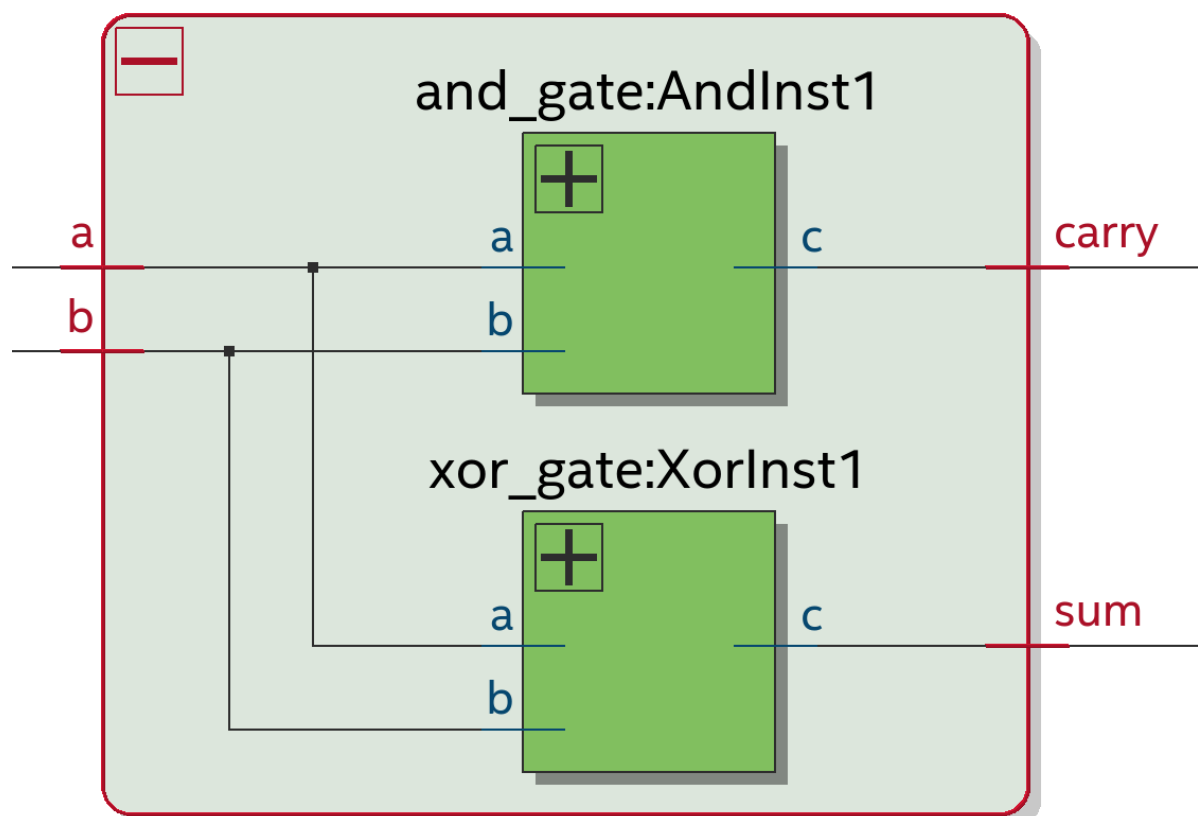

1-bit full adder

Component

2 1-bit Half Adder, 1 Or gate

Description

- 3 Inputs: two bits (A , B) , one bit (Cin)
- 2 Outputs: one bit (Sum), one bit (Cout)

Idea

- A and B were made the input of the 1st half adder.
- The output of this adder was made input of the 2nd half adder with Cin as the 2nd input
- The carry of the two half-adder were Or-ed to get the Cout of the full adder

$\text{Sum} = A \text{ xor } B \text{ xor } \text{Cin}; \quad \text{Cout} = A.B + B.\text{Cin} + A.\text{Cin};$

A	B	Cin	Sum	Cout
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

